

# EE 5304 : POWER ELECTRONICS

## COMPUTER SIMULATION OF POWER ELECTRONIC CIRCUITS

NAME : MAHINDAPALA D. P. P.

REG NO : EG/2016/2916

GROUP NO : EE 12


DATE : 30/08/2019

**DATE** : **23/08/2019**


**EXPERIMENT** : **COMPUTER SIMULATION OF**  
**POWER ELECTRONIC CIRCUITS**

**OBSERVATIONS** :

### **PART 01**

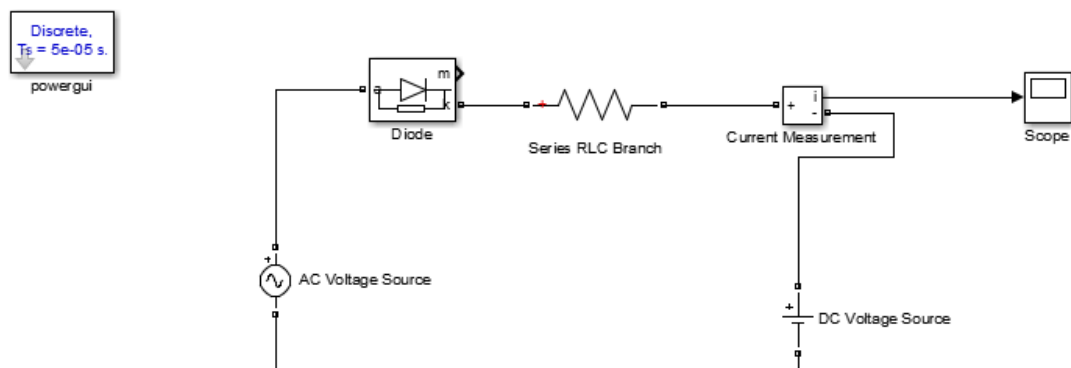

**FIGURE 1 : MATLAB SIMULATION CIRCUIT**

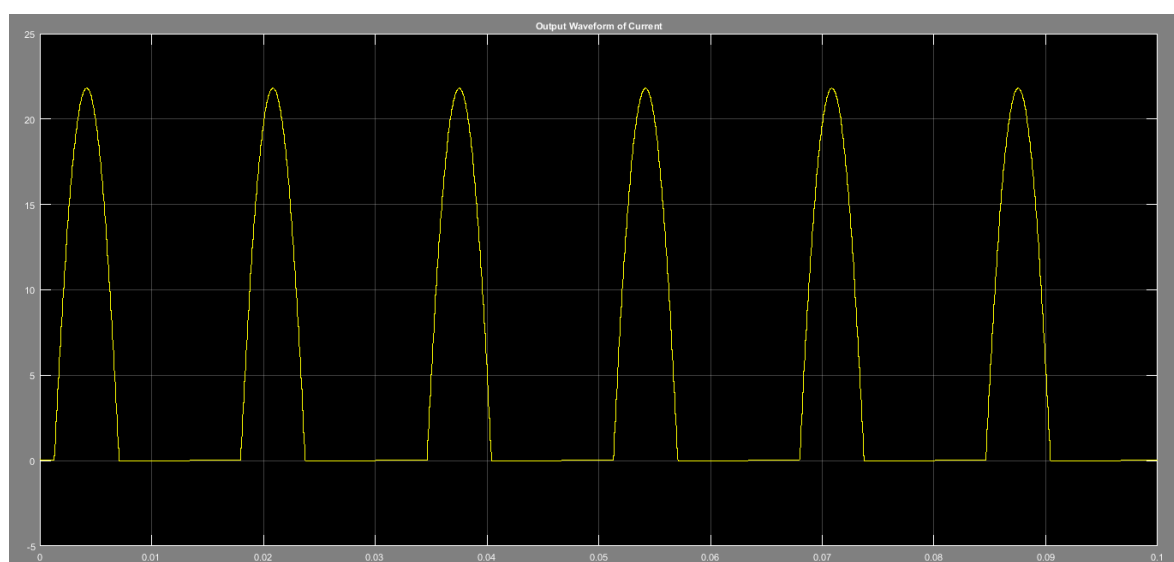

**FIGURE 2 : OUTPUT WAVEFORM OF CURRENT**

## PART 02

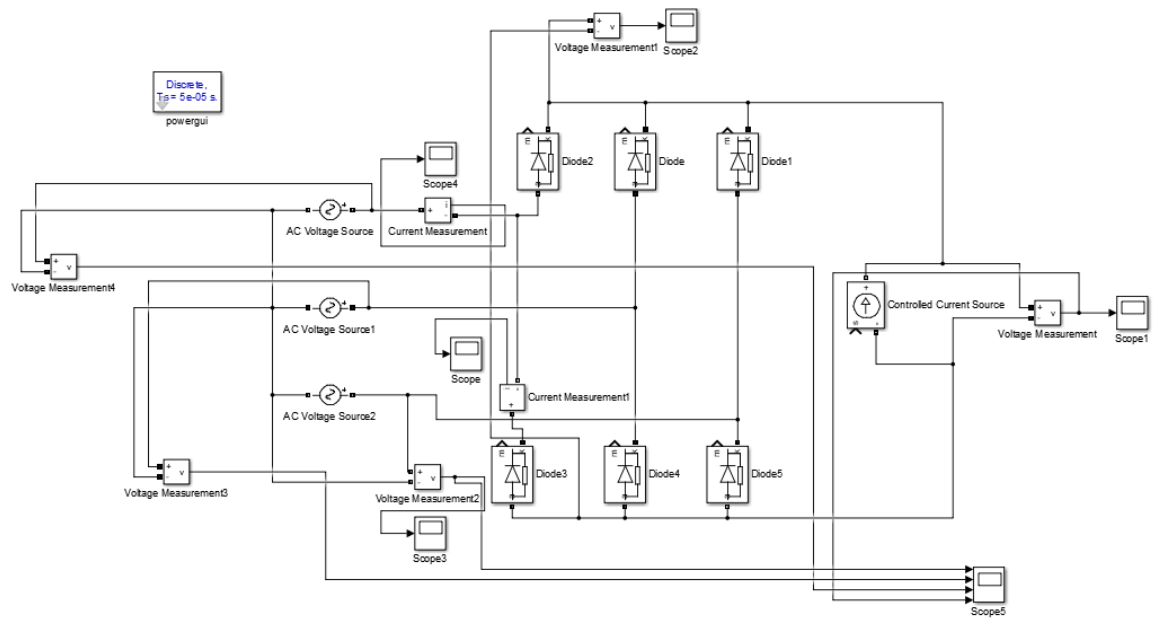


FIGURE 3 : MATLAB SIMULATION CIRCUIT

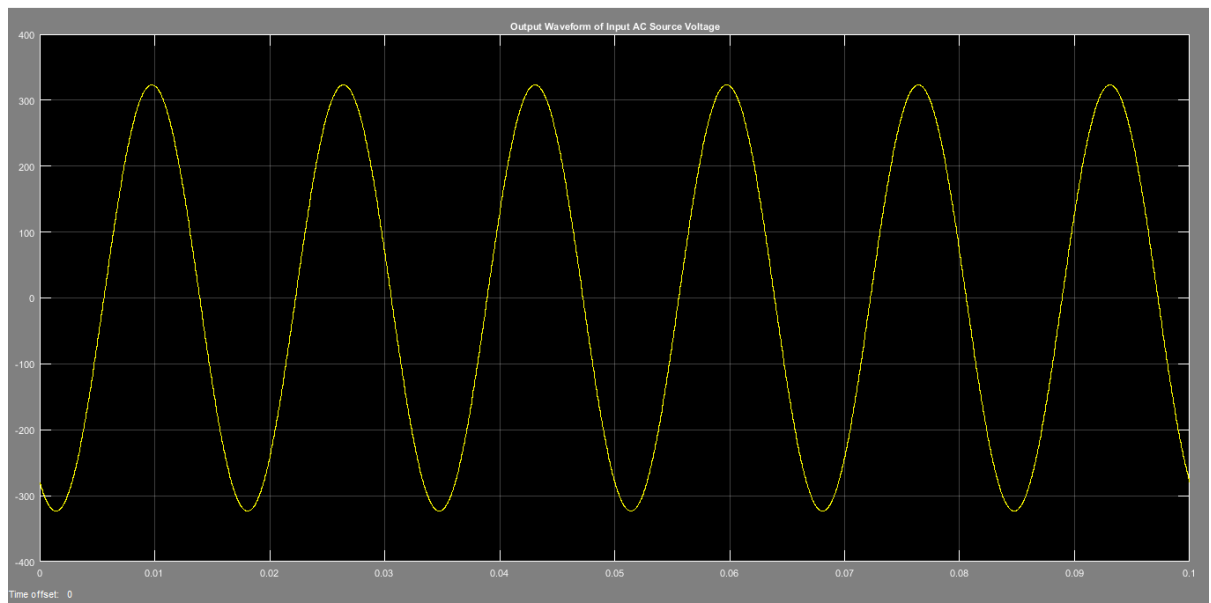


FIGURE 4 : INPUT AC SOURCE VOLTAGE

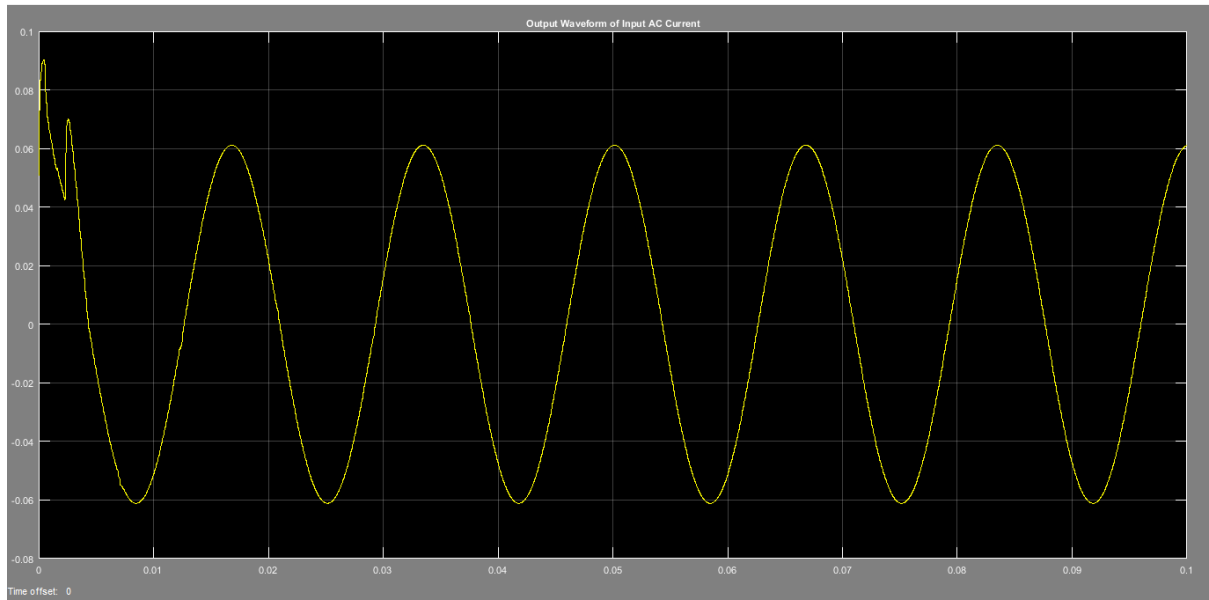


FIGURE 5 : INPUT AC CURRENT

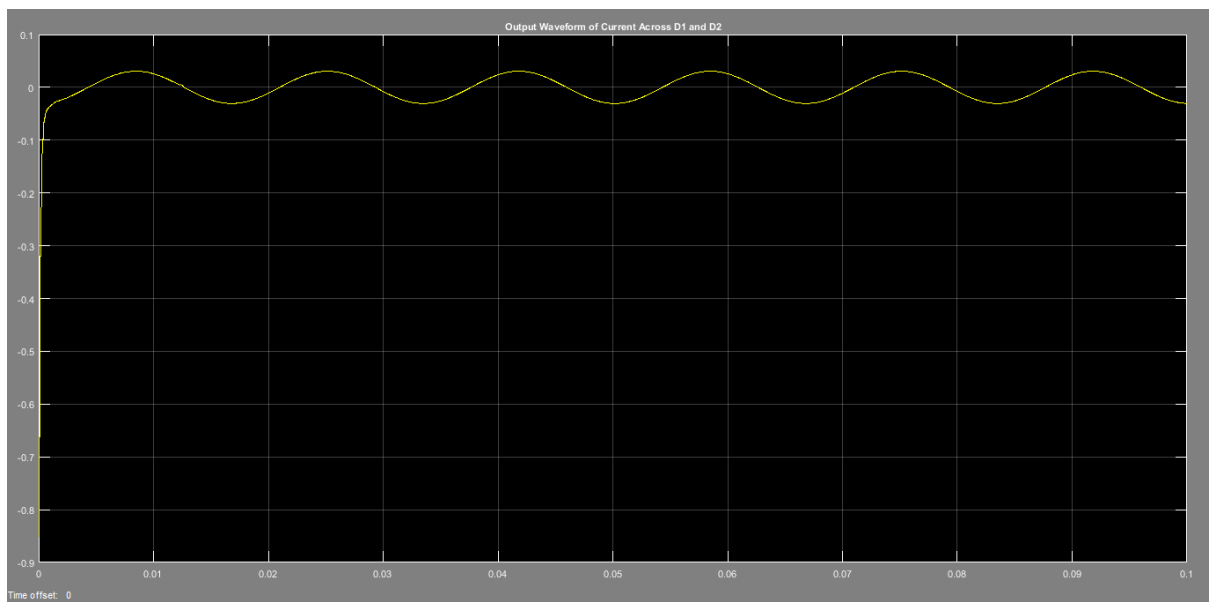


FIGURE 6 : CURRENT ACROSS DIODE D1 AND D2

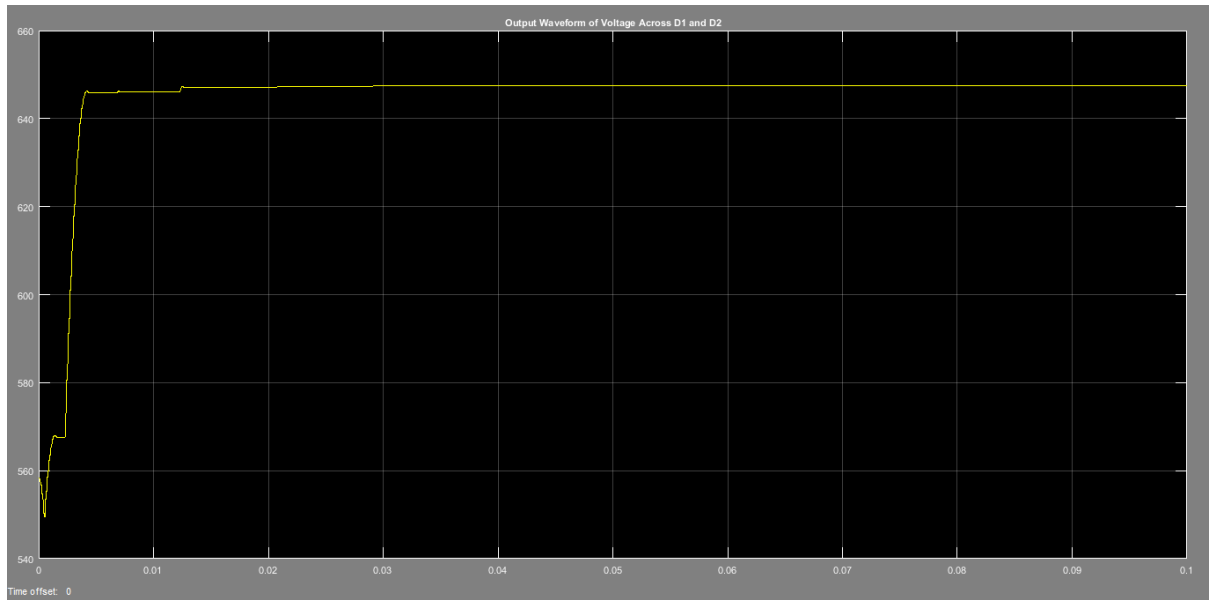


FIGURE 7 : VOLTAGE ACROSS DIODE D1 AND D2



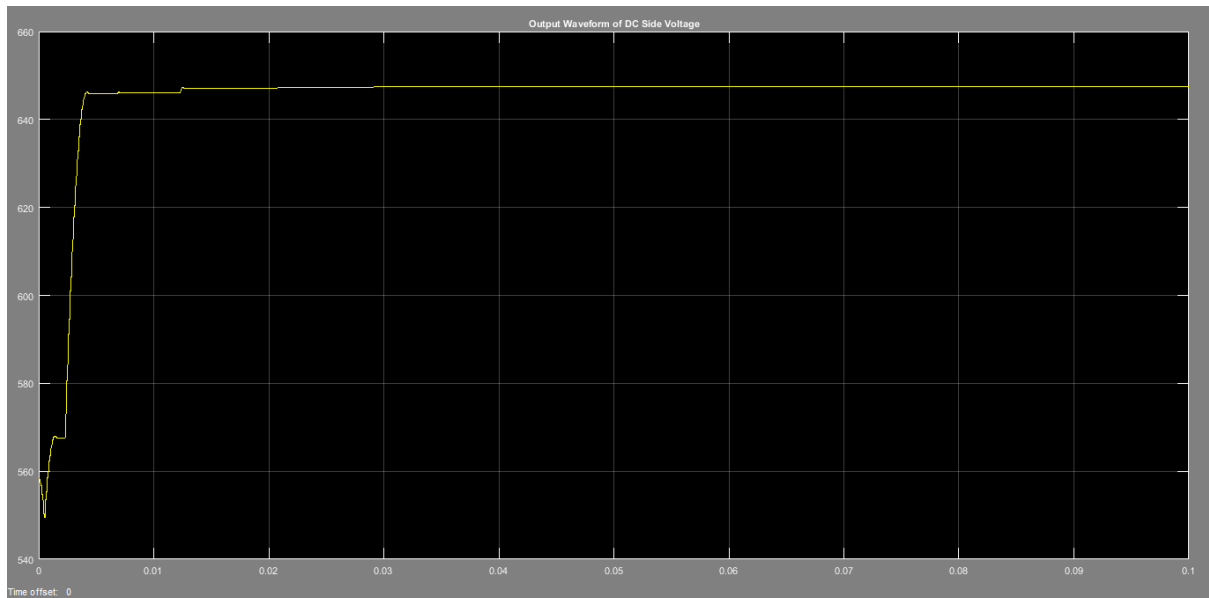


FIGURE 8 : DC SIDE VOLTAGE

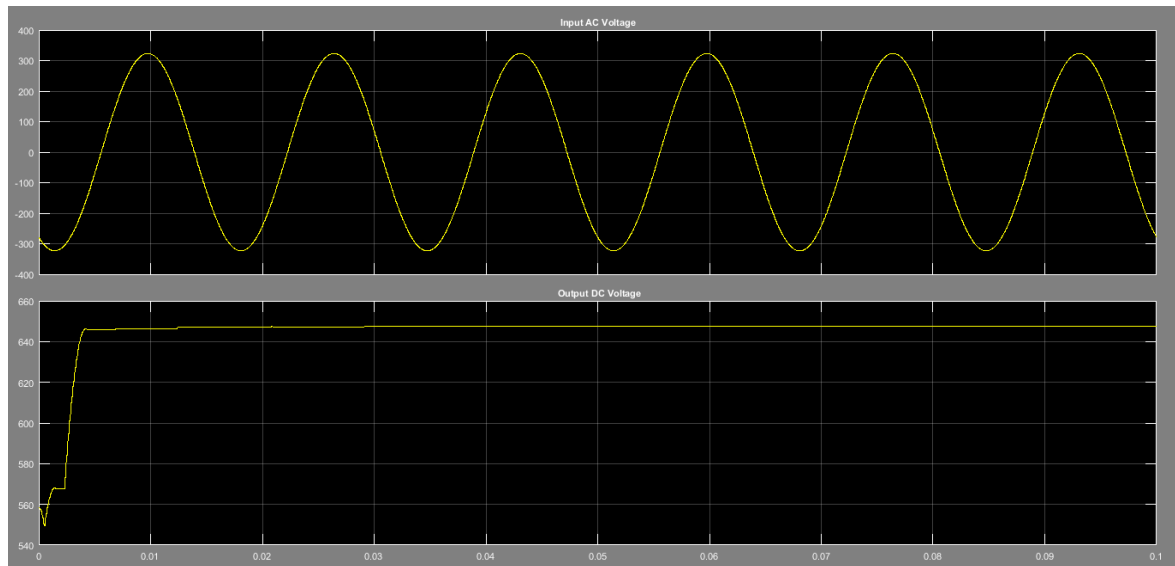

**FIGURE 9 : INPUT AC VOLTAGE AND OUTPUT DC VOLTAGE**

### **PART 03**

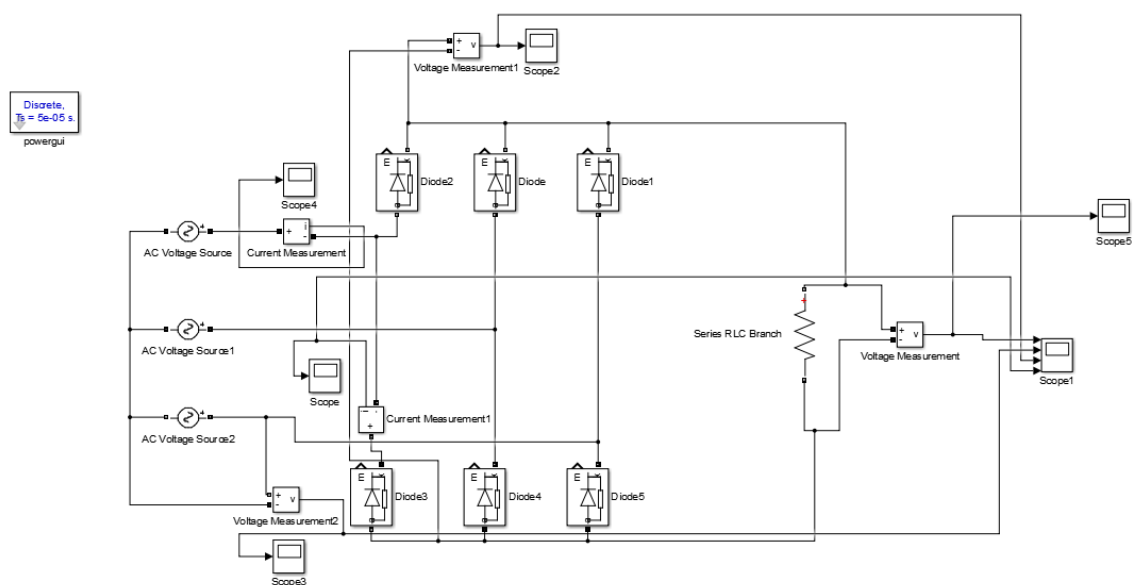

**FIGURE 10 : MATLAB SIMULATION CIRCUIT**

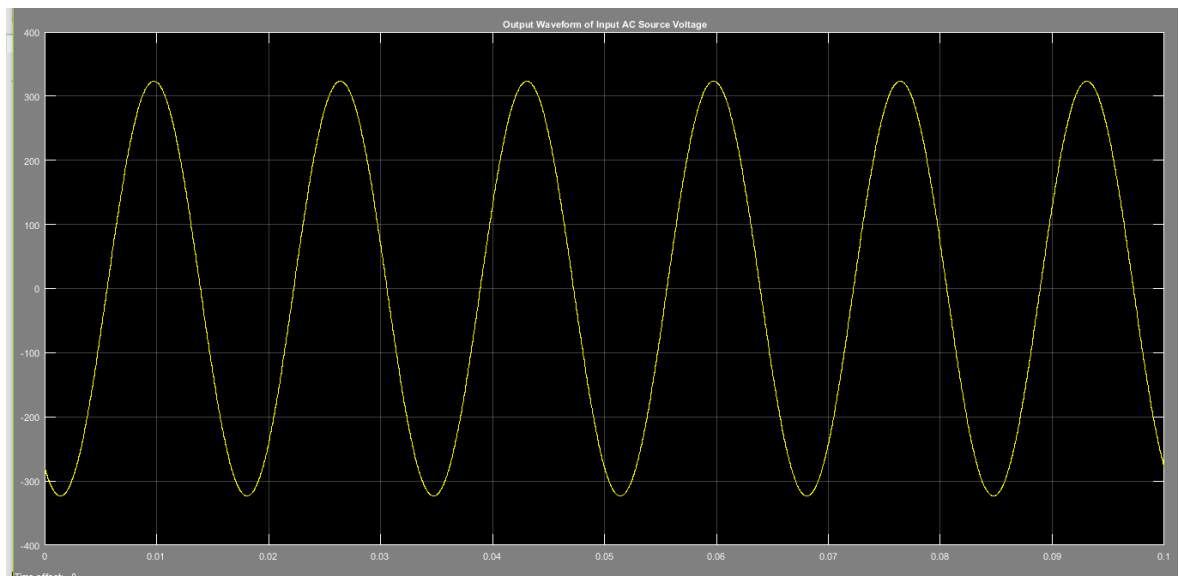


FIGURE 11 : INPUT AC SOURCE VOLTAGE

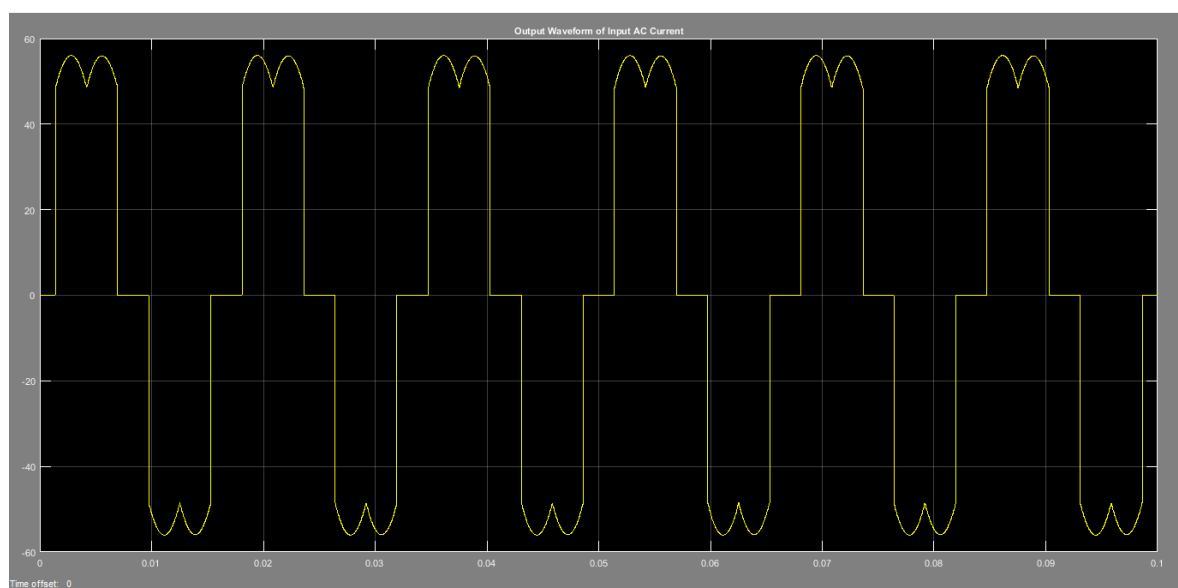


FIGURE 12 : INPUT AC CURRENT

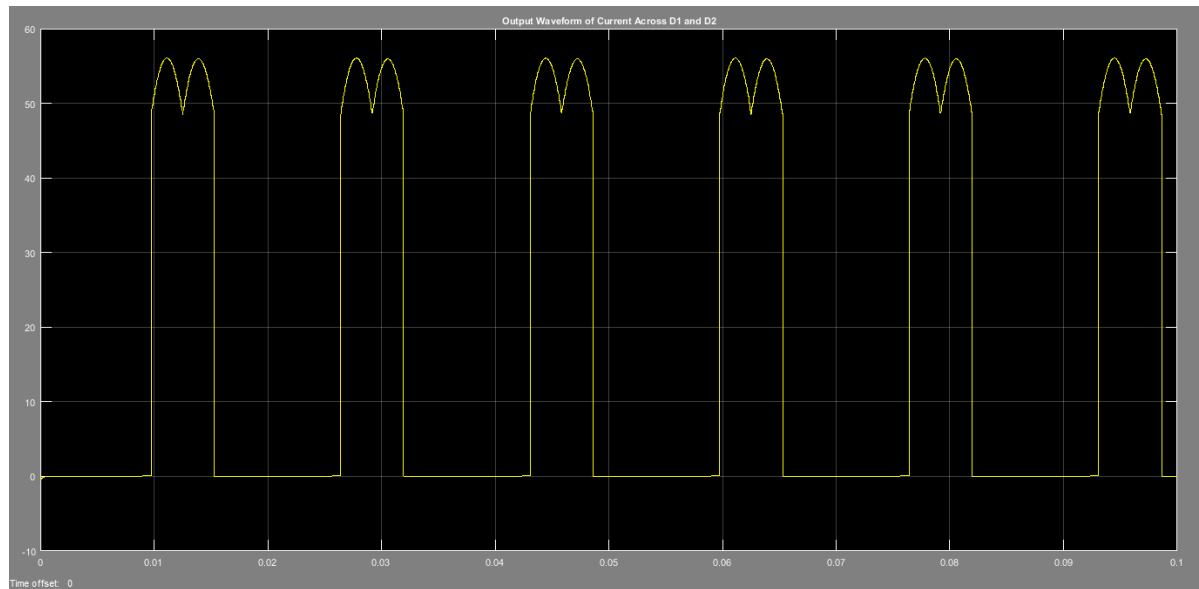


FIGURE 13 : CURRENT ACROSS DIODE D1 AND D2

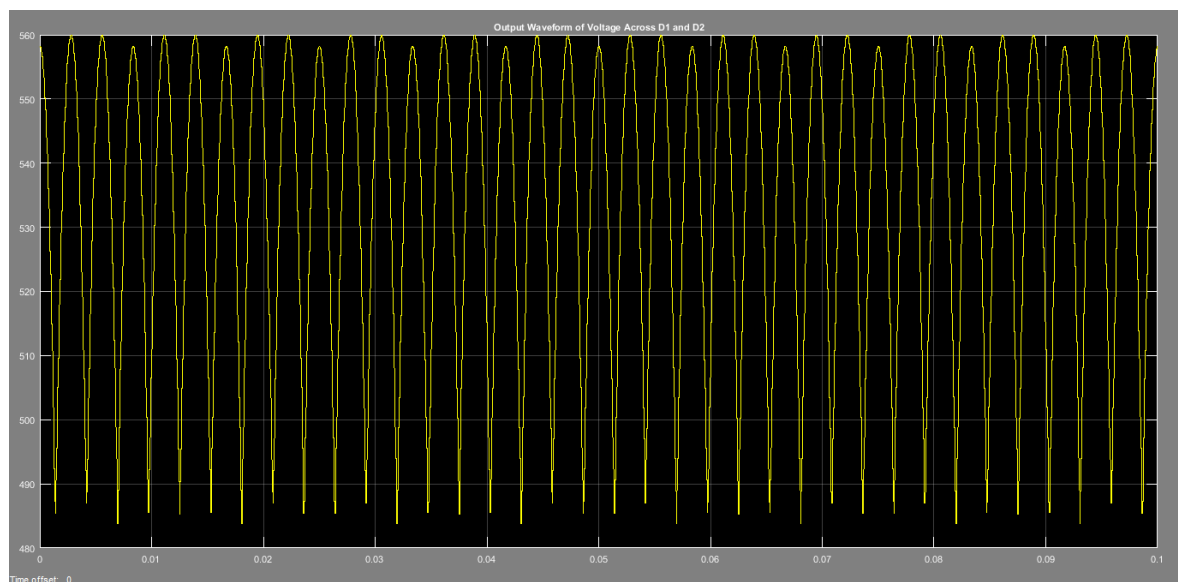


FIGURE 14 : VOLTAGE ACROSS DIODE D1 AND D2



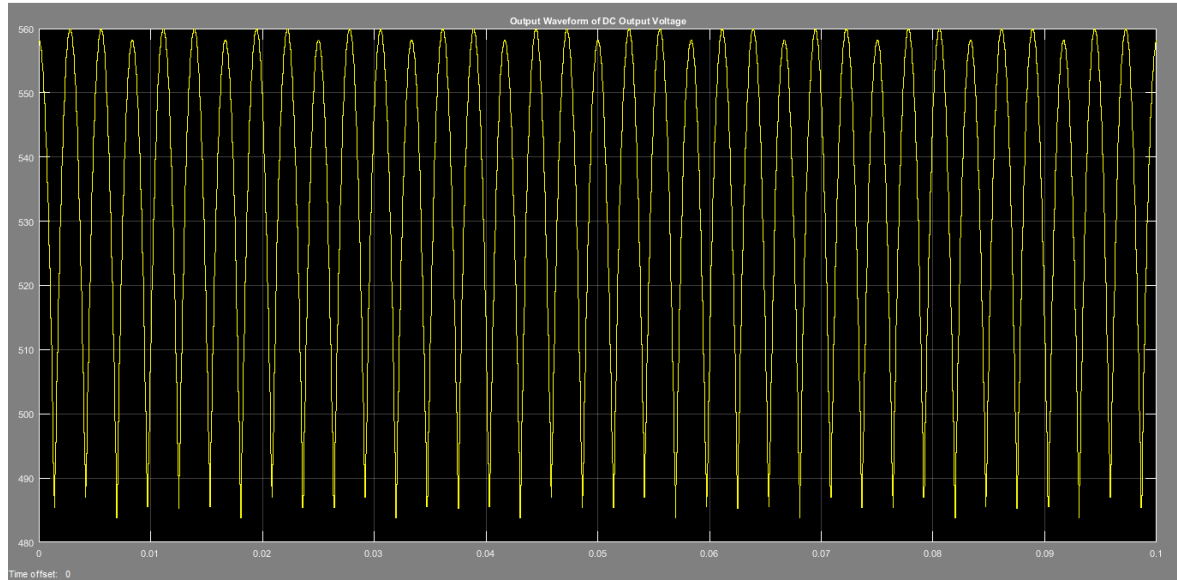


FIGURE 15 : DC SIDE VOLTAGE

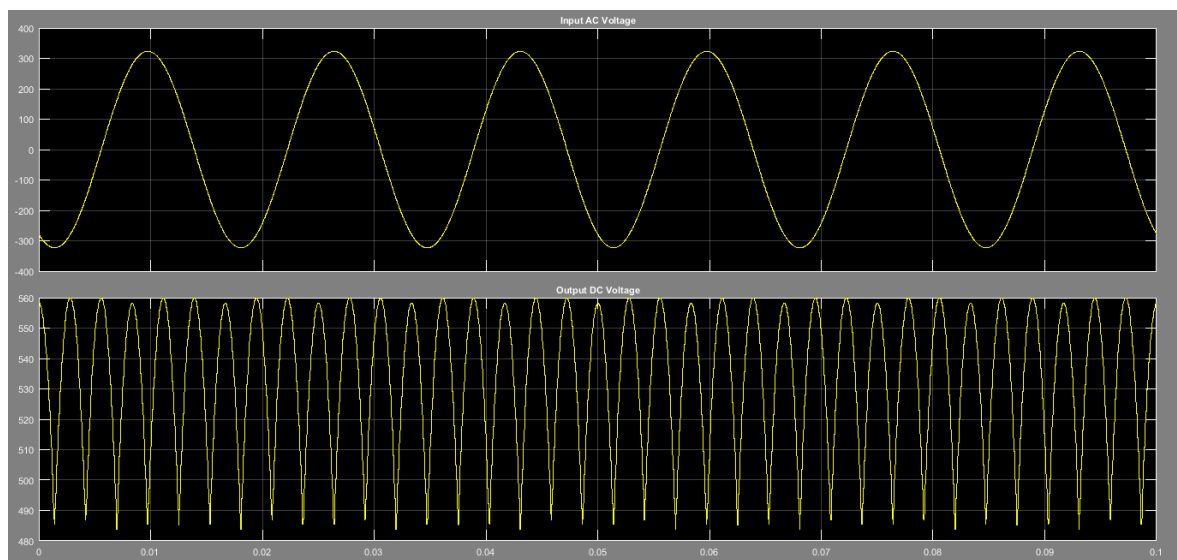


FIGURE 16 : INPUT AC VOLTAGE AND OUTPUT DC VOLTAGE